

Home Assignment

43)

[CO-2]

- ① @ The current in a circuit is given by $I = 40 \sin(628)t$
 Calculate i) Frequency ii) RMS Value iii) Average value iv) Form F.
 v) Peak factor.

Sol. Given, $I = 40 \sin(628)t$

i) General form $I = A \sin(2\pi ft)$

$$2\pi f = 628$$

$$f = \frac{628}{2\pi} = \frac{628}{2 \times 3.14} \Rightarrow \text{frequency (f)} = \underline{100 \text{ Hz}}$$

ii) RMS Value:

For a sinusoidal function $I = A \sin(\omega t)$

$$I_{\text{rms}} = \frac{A}{\sqrt{2}} = \frac{40}{\sqrt{2}}$$

$$\boxed{I_{\text{rms}} = 28.28 \text{ A}}$$

iii) Average Value:

The average value of a sinusoidal function over one complete cycle is $I_{\text{avg}} = 0$. This is because the positive & Negative values over a cycle cancel each other out.

iv) Form Factor: The form factor is the ratio of RMS value to the average value.

$$\boxed{FF = \sqrt{2}}$$

v) Peak Factor: Peak F = $\frac{40}{I_{\text{rms}}} = \frac{40}{28.28} = \underline{\underline{1.414}}$.

⑥ Write the polar form of the Voltage given by $V(t) = \sin(50\pi t + \pi/3)$ V obtain its rectangular form?

sol: The polar form of a sinusoidal Voltage is:

$$V(t) = A \sin(\omega t + \phi)$$

but given $V(t) = \sin(50\pi t + \pi/3)$ V.

$$A = 1$$

$$\omega = 50\pi$$

$$\phi = \pi/3$$

$$V(t) = A \sin(\omega t + \phi) = A(\cos(\phi) + j \sin(\phi))$$

$$V(t) = 1(\cos(\pi/3) + j \sin(\pi/3))$$

$$\boxed{V(t) = \frac{1}{2} + j \frac{\sqrt{3}}{2}} \text{ (Rectangular form of the Voltage)}$$

⑦ The current drawn by a pure capacitance of $50 \mu\text{F}$ is 1.642 A from 220 V ac supply, find the supply frequency.

sol: Given, $I = 1.642$ A, $V = 220$ V, $C = 50 \mu\text{F}$

$$\text{We know } X_c = \frac{1}{2\pi f C} \rightarrow f = \frac{1}{2\pi X_c C}$$

$$f = \frac{1}{2 \times 1.642 \times 3.14 \times 10^{-6} \times 50 \times 10^{-6}}$$

$$f = \frac{1}{0.000163}$$

$$f \approx 6135.58 \text{ Hz}$$

\therefore The Supply frequency is approximately 6135.58 Hz.

② Q A $200\mu\text{F}$ Capacitor is connected across is 240V , 50Hz System Determine i) The Capacitance reactance ii) R.M.S Value of current iii) Equations for Voltages and currents?

Sol: i) $X_c = \frac{1}{2\pi f c}$

$$= \frac{1}{2\pi (50 \times 200)}$$

$$= \frac{1}{2 \times 3.14 \times 50 \times 200 \times 10^{-6}}$$

$$X_c = 318.31 \Omega$$

ii) $I_{\text{rms}} = \frac{V}{X_c}$

$$I_{\text{rms}} = \frac{240}{318.31}$$

$$I_{\text{rms}} = 0.754 \text{ A}$$

iii) $I(t) = I_{\text{rms}} \sin(2\pi f t + \phi)$

$$V(t) = I_{\text{rms}} X_c \cos(2\pi f t + \phi)$$

Substitute the values $\rightarrow I(t) = 0.754 \sin(2\pi t(50) + \phi)$

$$V(t) = (0.754)(318.31) \cos(2\pi t(50) + \phi)$$

③ Calculate the form factor & peak factor of a triangular wave in which the voltage rises uniform from 0 to 1V volts its time T seconds & completes the cycle by instant fall back to zero?

Sol: $V_{\text{rms}} = \frac{V_{\text{peak}}}{\sqrt{3}}$

Given 0 to 1V, so peak = 1

$$V_{\text{rms}} = \frac{1}{\sqrt{3}}$$

$$V_{avg} = \frac{V_{peak}}{2} = \frac{1}{2}$$


$$\text{Form factor (F.F)} = \frac{V_{rms}}{V_{avg}} = \frac{\frac{1}{\sqrt{3}}}{\frac{1}{2}} = \frac{2}{\sqrt{3}}$$

$$\boxed{F.F = 1.155}$$

$$\text{Peak factor} = \frac{V_{peak}}{V_{rms}} = \frac{1}{\frac{1}{\sqrt{3}}} = \frac{\sqrt{3}}{1} = \sqrt{3} = 1.732$$

$$\boxed{P.F = 1.732}$$

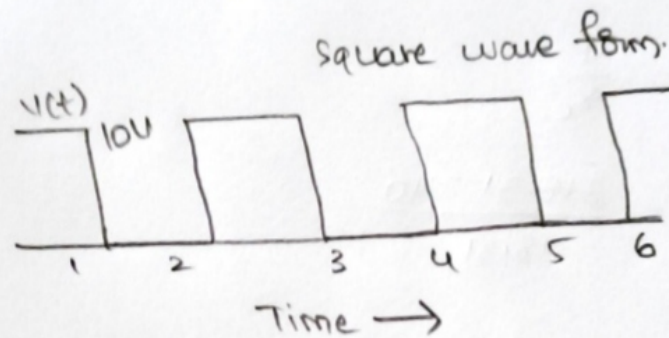Q Calculate the average & RMS values of the square wave.



sol:

$$v(t) = 10 \text{ for } 0 < t < 1$$

$$0 \text{ for } 1 < t < 2$$

$$V_{rms} = \sqrt{\frac{\int_0^2 (v^2(t)) dt}{2}} = \sqrt{\frac{\int_0^1 (10)^2 dt}{2}}$$

$$\boxed{V_{rms} = 7.071 \text{ V}}$$

$$V_{avg} = \frac{\int_0^2 v(t) dt}{2} = \frac{\int_0^1 10 dt}{2}$$

$$\boxed{V_{avg} = 5}$$